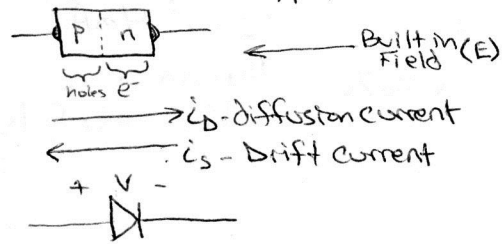


Group III w/3 → type n-semiconductor
Group IV w/3 → type p-semiconductor




$$I_D = I_S (e^{V_D/V_T} - 1) = \text{PNL}$$

$$V_T = \frac{KT}{q} = 25 \text{ mV @ room temp.}$$

Reverse Bias: $I_D \ll I_S$

Forward Bias: $I_D \gg I_S$

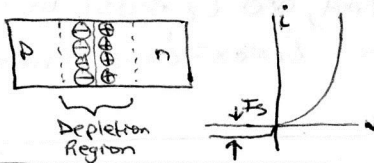

Piecewise Linear Diode Models (PNL)


$$I_D = I_S (e^{V_D/V_T} - 1) : \text{Normal Diodes}$$

V_D/V_F are the turn on voltages.

$$r_D = nV_T / I_D$$

Rectifier Circuits

Half-Wave Rectifier:

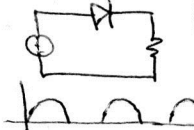

Full-Wave Rectifier:



$$\text{DC voltage} = V_{pk} + \frac{1}{2} V_{\text{ripple}}$$

$$V_D / V_F \approx 0.7 \text{ volts (Depending)}$$

half wave rectifier:


$$C = \frac{1}{f R_{Lmin} (V_r/V_p)} = \frac{I_{Lmax}}{f V_r}$$

Full wave rectifier:

$$C = \frac{1}{2 f R_{Lmin} (V_r/V_p)} = \frac{I_{Lmax}}{2 f V_r}$$

PIV rating is most voltage without a fatal Breakdown.

Voltage Doubler:

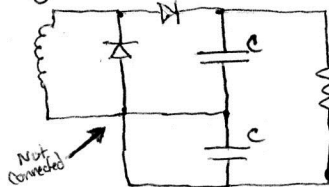

Peak Diode Current

$$I_{Lmax} = I_L (1 + 2\pi \sqrt{2} V_p / V_r)$$

$$I_{Lmax} = I_L (1 + 2\pi \sqrt{2} V_p / 2V_r)$$

$$\% \text{ ripple} = 100 \frac{V_{\text{ripple}}}{V_{D \text{ avg.}}}$$

$$\frac{V_{\text{ripple}}}{V_{\text{peak}}} = \frac{T}{2 R_L C}$$

$$I_S = \frac{V_C - V_Z}{R_S} \quad \text{finding } R_S \text{ (Zener rect.)}$$

$$V_C = V_{sec} - 2V_F$$

$$I_S = I_{Zmin} + I_{Lmax} \text{ (} R_{Lmax} \text{ value)}$$

$$R_S = \frac{V_{sec} - 2V_F - V_Z}{I_{Zmin} + I_{Lmax}}$$

$$P_{Zmax} = V_Z I_S$$

$$C_{min} = \frac{I_S}{2 f (V_C - V_Z)}$$

Caps ss for AC voltage
Caps oc for DC voltage


$$X_C = \text{reactance} = -\frac{1}{2\pi f C}$$

Capacitor Reactance for an attenuator

Zener Diodes

clamp the voltage at or below a certain level.

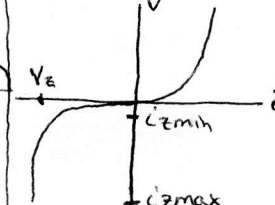
Convert to higher freq, then smaller transformer.



I_{Zmax} determined by max power dissipation rating.

if too big then reverse breakdown

voltage regulator:

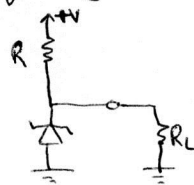

$$R_{max}$$

$$I_{Zmin}$$

$$I_{Zmax}$$

$$I_{Lmax} < 0.5 P_{Zmax} / V_Z$$

2x safe for Zener power

$$R_{min}$$

$$I_{Zmax} \text{ (all current)}$$

Rule of Thumbs

V_{sec} is 30-50% higher V_L

I_{Zmin} is $1/20 I_{Zmax}$


Cap used is $5 \times C_{min}$

make power diss. $1/2 P_{max}$

Separate AC/DC analysis: Superposition
Caps sc for AC
Caps oc for DC

DC V & i is much higher than AC

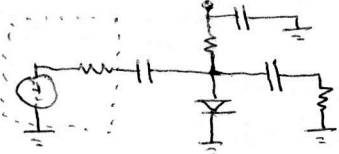Design path $\rightarrow r_D$ values $\rightarrow I_D$ values, Bias resistor values.



AC analysis, current all through r_D , solve for r_D .

After find r_D , use $r_D = \frac{nV_T}{I_D}$ to find I_D .
use these I_D values to find R_B using DC.

Inductors Block AC, Pass DC

Capacitors Block DC, Pass AC

Varactor & Schottky Diodes

Varactor diode:

voltage Variable Capacitor (VVC)

std. Pn-junction under reverse bias

$$C = \epsilon A / d \text{ (dielectric const) (Area) / sep. dist.}$$


Schottky Diode:

Low forward voltage

voltage clamping.


Fast switching time

PNL model of a diode

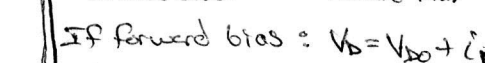

$$\text{If forward bias: } V_D = V_{D0} + I_D r_D$$

Voltage regulator

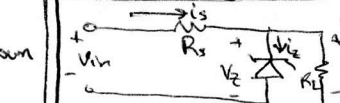

$$R_{max} = \frac{V_{inmin} - V_Z}{I_{Zmin}} = \frac{V_{inmin} - V_Z}{I_{Zmin} + I_{Lmax}}$$

$$R_{min} = \frac{V_{inmax} - V_Z}{I_{Zmax}}$$


$$R_{min} < R < R_{max} \text{ (we hope at least)}$$

If this isn't true, probably too small of a Zener diode for the size of the load

PNL i_v characteristics


$$r_D = \frac{1}{\text{slope of line}} \quad \frac{I}{V} = \frac{\Delta V}{\Delta I}$$

V_F is the horizontal intercept (x-int)

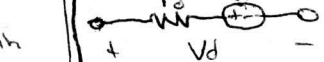


Give reason's not to use large Caps to make very small ripple voltages:

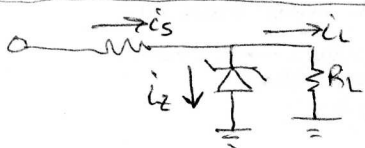- 1) relatively expensive as size increases
- 2) Take up a lot of space and are heavy




For Full-wave rect (only 2 diodes) if one installed backwards then no current gets to the load, $V_o = 0$

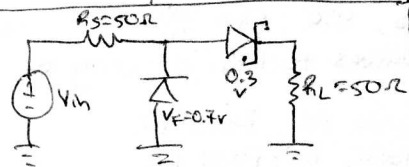The max i_L value must also be able to go through the Zener. The Zener power should be $V_Z(i_{Lmax}) = P_{Zer}$ with safety factor $\times 2$




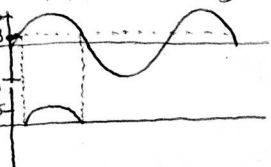When $V_{in} > 0.3V$ for shottkey, the voltage in excess over $0.3V$ is divided up over both resistors as a percent. In this case, evenly. Thus, the following occurs:



goes to 0.35 cause max diff is $0.7V$. It's divided up evenly across R_s .

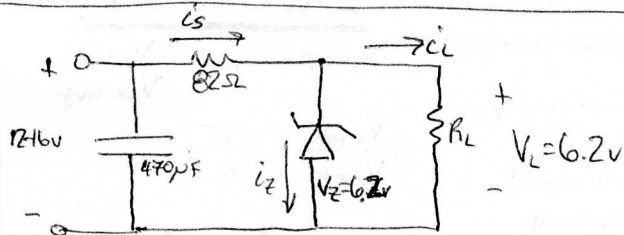Zener works like normal diode in fwd bias



$i_{Zmin} = 4mA$
How large i_L until Zener fails.

If $V_Z = 6.2V$,

$$i_{smin} = \frac{V_{emh} - V_Z}{82\Omega} = \frac{12 - 6.2}{82} = 70.7mA$$

$$i_{smax} = \frac{V_{max} - V_Z}{82\Omega} = \frac{16 - 6.2}{82} = 119.5mA$$

$$i_s = i_Z + i_L$$

i_s can be as low as $70.7mA$, and i_Z must be $\geq 4mA$, so i_L can be no larger than: $i_{Lmax} = i_{smin} - i_{Zmin} = 70.7 - 4 = 66.7mA$

negligible ripple means diode on. ripple significant means the diode is off and cap. is discharging.